
 


# SYNCHRONOUS LOGIC

 


- 1) Sequential Logic
- 2) Synchronous Design
- 3) Synchronous Timing Analysis
- 4) Single Clock Design
- 5) Finite State Machines
- 6) Mealy and Moore
- 7) State Transition Diagrams





# ROAD TRAVELED SO FAR..

 

## Combinational contract:

- Voltage-based "bits"
- 1-bit per wire
- Generate quality outputs, tolerate inferior inputs
- Combinational contract
- Complete in/out/timing spec

## Acyclic connections

### Composable blocks

### Design:

- truth tables
- sum-of-products
- muxes
- ROMs

## Storage & state

### Dynamic discipline

### Finite-state machines


- Throughput & latency
- Pipelining

Our motto: Sweat the details once, and then put a box around it!


 
# SOMETHING WE CAN'T BUILD

What if you were given the following system design specification?




What makes this System so different from those we've discussed before?

1. "State" - i.e. the circuit has memory
2. The output was changed by a input "event" (pushing a button) rather than an input "value"




# "SEQUENTIAL" = STATEFUL

 


Plan: Build a Sequential Circuit with stored digital STATE -

- MEMORY stores CURRENT state
- Combinational Logic computes
  - the NEXT state (Based on inputs & current state)
  - the OUTPUTs (Based on inputs and/or current state)
  - State changes on LOAD control input

 Didn't we develop some memory devices last time?



# "SYNCHRONOUS" SINGLE-CLOCK LOGIC

 


Questions for register-based designs:

- How much time for useful work (i.e. for combinational logic delay)?

- Does it help to guarantee a minimum  $t_{CD}$ ? How 'bout designing registers so that

$$t_{CD,reg} \geq t_{HOLD,reg}?$$

 - What happens if CLK signal doesn't arrive at the two registers at exactly the same time (a phenomenon known as "clock skew")?




$$t_1 = t_{CD,reg1} + t_{CD,L} \geq t_{HOLD,reg2}$$

$$t_2 = t_{PD,reg1} + t_{PD,L} \leq t_{CLK} - t_{SETUP,reg2}$$

$$\text{Minimum Clock Period : } t_{CLK} \geq t_{PD,reg1} + t_{PD,L} + t_{SETUP,reg2}$$



# EXAMPLE: SYNCHRONOUS TIMING

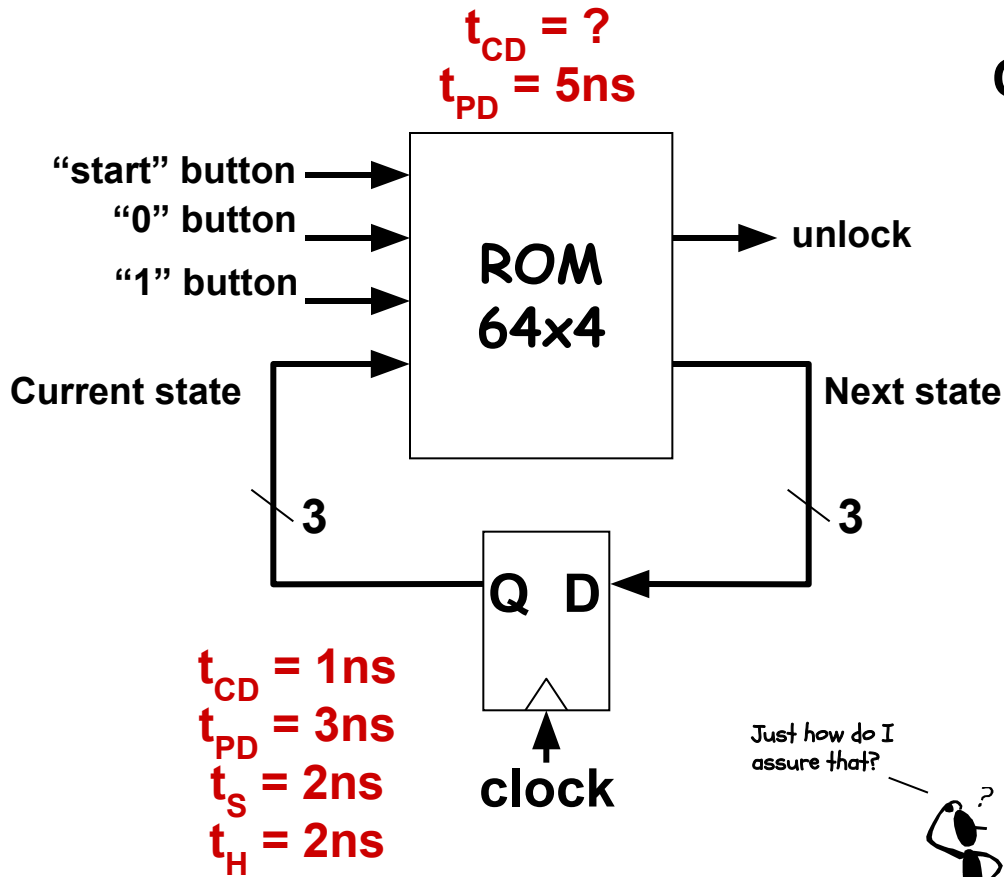

## Questions:

### 1. $t_{CD}$ for the ROM?

$$t_{CD,REG} + t_{CD,ROM} > t_{H,REG}$$

$$1 ns + t_{CD,ROM} > 2 ns$$

$$t_{CD,ROM} > 1 ns$$

### 2. Min. clock period?

$$t_{CLK} > t_{PD,REG} + t_{PD,ROM} + t_{S,REG}$$

$$t_{CLK} > 3 ns + 5 ns + 2 ns$$

$$t_{CLK} > 10 ns$$

### 3. Constraints on inputs?

“start”, “0”, and “1” must be valid

$t_{PD,ROM} + t_{S,REG} = 5 + 2 = 7 ns$   
before the clock and held

$t_{H,REG} - t_{CD,ROM} = 2 - 1 = 1 ns$   
after it.

Just how do I  
assure that?



 
# SYNCHRONOUS SINGLE-CLOCK DESIGN



Sequential  $\neq$  Synchronous

However, Synchronous = A recipe for robust sequential circuits:



- No combinational cycles  
(other than those already inside the registers)
- Only cares about values of combinational circuits just before rising edge of clock
- Clock period greater than every combinational delay
- Changes state after all logic transitions have stopped!



# DESIGNING SEQUENTIAL LOGIC

Sequential logic is used when the solution to some design problem involves a *sequence of steps*:

How to open digital combination lock w/ 3 buttons ("start", "0" and "1"):

Step 1: press "start" button

Step 2: press "0" button


Step 3: press "1" button

Step 4: press "1" button

Step 5: press "0" button



 Information remembered between steps is called **state**. Might be just what step we're on, or might include results from earlier steps we'll need to complete a later step.







# IMPLEMENTING A "STATE MACHINE"

This flavor of "truth-table" is called a "state-transition table"


This is starting to look like a PROGRAM




Current State					Next State		
	"start"	"1"	"0"		unlock		
---		1	---	---	start	0	000
start	000	0	0	1	digit1	0	001
start	000	0	1	0	error	0	101
start	000	0	0	0	start	0	000
digit1	001	0	1	0	digit2	0	010
digit1	001	0	0	1	error	0	101
digit1	001	0	0	0	digit1	0	001
digit2	010	0	1	0	digit3	0	011
...							
digit3	011	0	0	1	unlock	0	100
...							
unlock	100	0	1	0	error	1	101
unlock	100	0	0	1	error	1	101
unlock	100	0	0	0	unlock	1	100
error	101	0	---	---	error	0	101

6 different states → encode using 3 bits

# NOW, WE DO IT WITH HARDWARE!

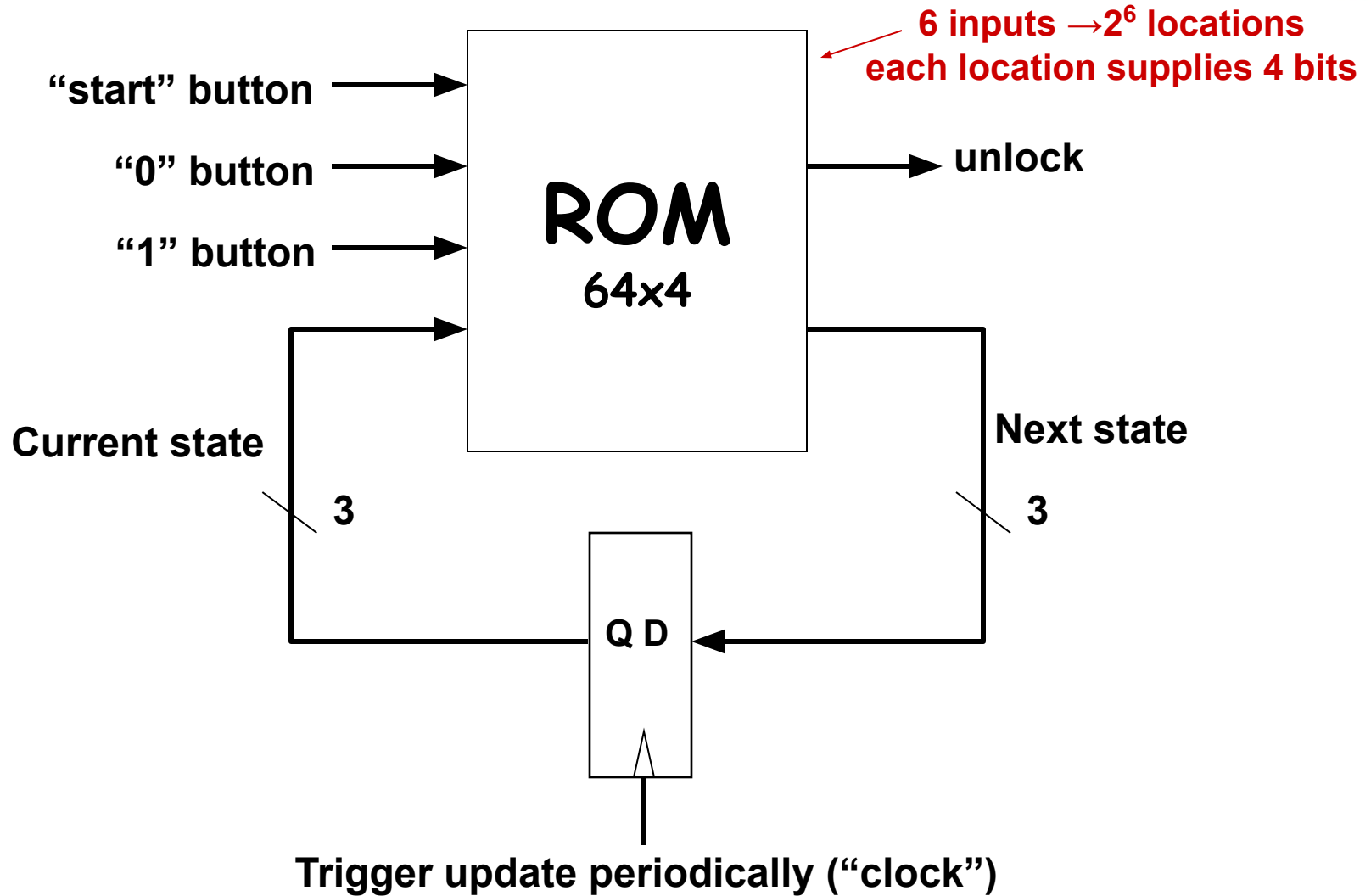

# A FINITE STATE MACHINE

 


## A Finite State Machine has:

- $k$  States  $S_1, S_2, \dots, S_k$  (one is the “initial” state)
- $m$  inputs  $I_1, I_2, \dots, I_m$
- $n$  outputs  $O_1, O_2, \dots, O_n$
- Transition Rules,  $S'(S_i, I_1, I_2, \dots, I_m)$   
for each state and input combination
- Output Rules,  $O(S_i)$  for each state



# DISCRETE STATE, DISCRETE TIME

 


While a ROM is shown here in the feedback path any form of combinational logic can be used to construct a state machine.

Two design choices:

 
- (1) outputs *only* depend on state (Moore)
- (2) outputs depend on inputs + state (Mealy)

$s$  state bits  $\rightarrow 2^s$  possible states






# STATE TRANSITION DIAGRAMS

 


A state transition diagram is an abstract "graph" representation of a "state transition table", where each state is represented as a node and each transition is represented as an arc. **It represents the machine's behavior not its implementation!**

★ = no buttons pressed

 




# EXAMPLE STATE DIAGRAMS

 

MOORE Machine:  
Outputs on States

 

MEALY Machine:  
Outputs on Transitions

Arcs leaving a state must be:

(1) **mutually exclusive**

can only have one choice for any given input value

(2) **collectively exhaustive**

every state must specify what happens for each possible input combination. "Nothing happens" means arc back to itself.

# NEXT TIME



Counting state machines

