


Binary Multipliers

The key trick of multiplication is memorizing a digit-to-digit table...

Everything else is just adding

×	0	1
0	0	0
1	0	1

×	0	1	2	3	4	5	6	7	8	9
0	0	0	0	0	0	0	0	0	0	0
1	0	1	2	3	4	5	6	7	8	9
2	0	2	4	6	8	10	12	14	16	18
3	0	3	6	9	12	15	18	21	24	27
4	0	4	8	12	16	20	24	28	32	36
5	0	5	10	15	20	25	30	35	40	45
6	0	6	12	18	24	30	36	42	48	54
7	0	7	14	21	28	35	42	49	56	63
8	0	8	16	24	32	40	48	56	64	72
9	0	9	18	27	36	45	54	63	72	81

 

You've got to be kidding... It can't be that easy

Have We Forgotten Something?

Our ALU can add, subtract, shift, and perform Boolean functions. But, even rabbits know how to multiply...



But, it is a huge step in terms of logic... Including a multiplier unit in an ALU doubles the number of gates used.

A good (compact and high performance) multiplier can also be tricky to design. Here we will give an overview of some of the tricks used.

Binary Multiplication

The "Binary" Multiplication Table

X	0	1
0	0	0
1	0	1

Hey, that looks like an AND gate



Binary multiplication is implemented using the same basic longhand algorithm that you learned in grade school.

$$\begin{array}{r} A_3 \quad A_2 \quad A_1 \quad A_0 \\ \times B_3 \quad B_2 \quad B_1 \quad B_0 \\ \hline \end{array}$$

$A_j B_i$ is a "partial product" \longrightarrow

$$\begin{array}{r} A_3 B_0 \quad A_2 B_0 \quad A_1 B_0 \quad A_0 B_0 \\ A_3 B_1 \quad A_2 B_1 \quad A_1 B_1 \quad A_0 B_1 \\ A_3 B_2 \quad A_2 B_2 \quad A_1 B_2 \quad A_0 B_2 \\ + A_3 B_3 \quad A_2 B_3 \quad A_1 B_3 \quad A_0 B_3 \\ \hline \end{array}$$


Multiplying N-digit number by M-digit number gives (N+M)-digit result

Easy part: forming partial products (just an AND gate since B_i is either 0 or 1)
 Hard part: adding M, N-bit partial products

Multiplying in Assembly

One can use this “Shift and Add” approach to write a multiply function in assembly language

```
# Multiplies unsigned arguments in $a0 and $a1
# and returns value in $v0 ignoring overflows
multu: addiu    $v0,$0,0      # zero product register
loop:  andi    $t1,$a0,1     # check low-order bit
      beq    $t1,$0,noadd   # do we need to add?
      add   $v0,$v0,$a1     # add multiplicand to product
noadd: srl    $a0,$a0,1     # multiplier / 2
      sll   $a1,$a1,1     # 2 * multiplicand
      bne   $a0,$0,loop    # keep adding if there are
      jr   $31
```

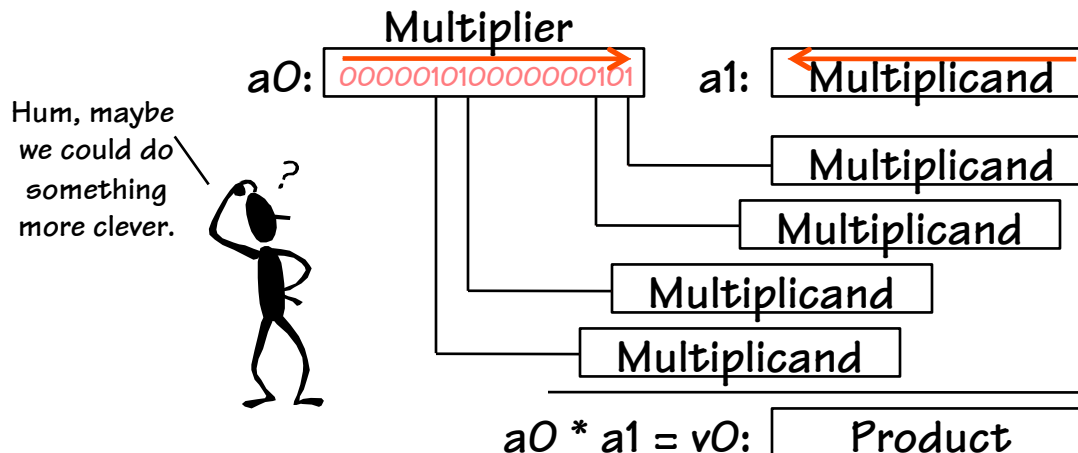

Multiplier Unit-Block



We introduce a new abstraction to aid in the construction of multipliers called the “Unsigned Multiplier Unit-block”

We did a similar thing last lecture when we converted our adder to an add/subtract unit.

A_k are bits of the Multiplicand and B_i are bits of the Multiplier.

The **PP** inputs and outputs represent “partial products” which are partial results from adding together shifted instances of the Multiplicand.

The initial PP_0 is zero.

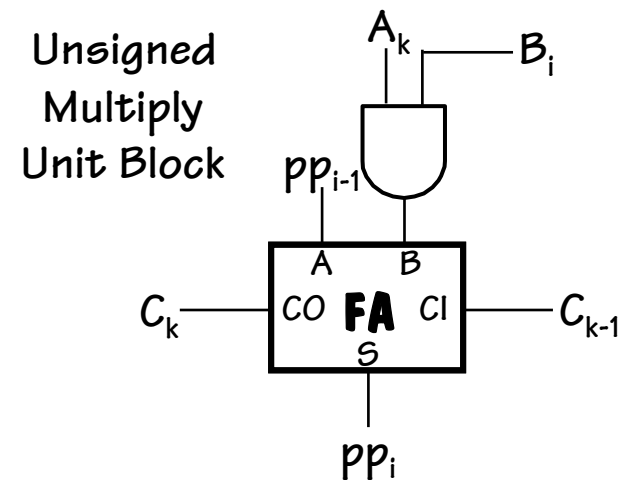 

Simple Combinational Multiplier

$$t_{PD} = 10 * t_{PD}$$




not 16

$$t_{PD} = (2*(N-1) + N) * t_{PD}$$

Components

$N * HA$

$N(N-1) * FA$

 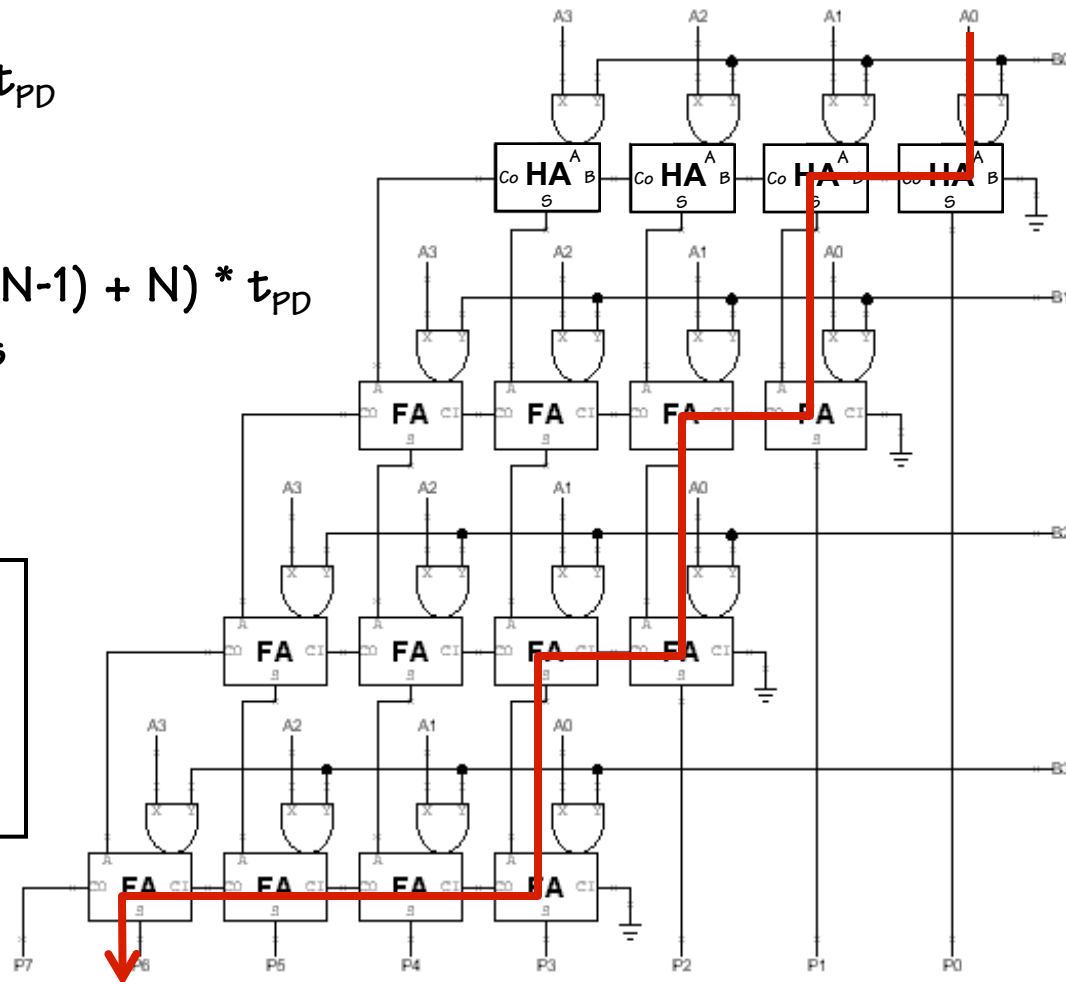 

To determine the timing specification of a composite combinational circuit we find the worst-case path for every output to any input.



NB: this circuit only works for nonnegative operands

"Carry-Save" Combinational Multiplier

Observation: Rather than propagating the carries to the next adder in each row, they can instead be forwarded to the next column of the following row


$$t_{PD} = 8 * t_{PD}$$

$$t_{PD} = (N+N) * t_{PD}$$

Components

~~N * FA~~

$N^2 * FA$

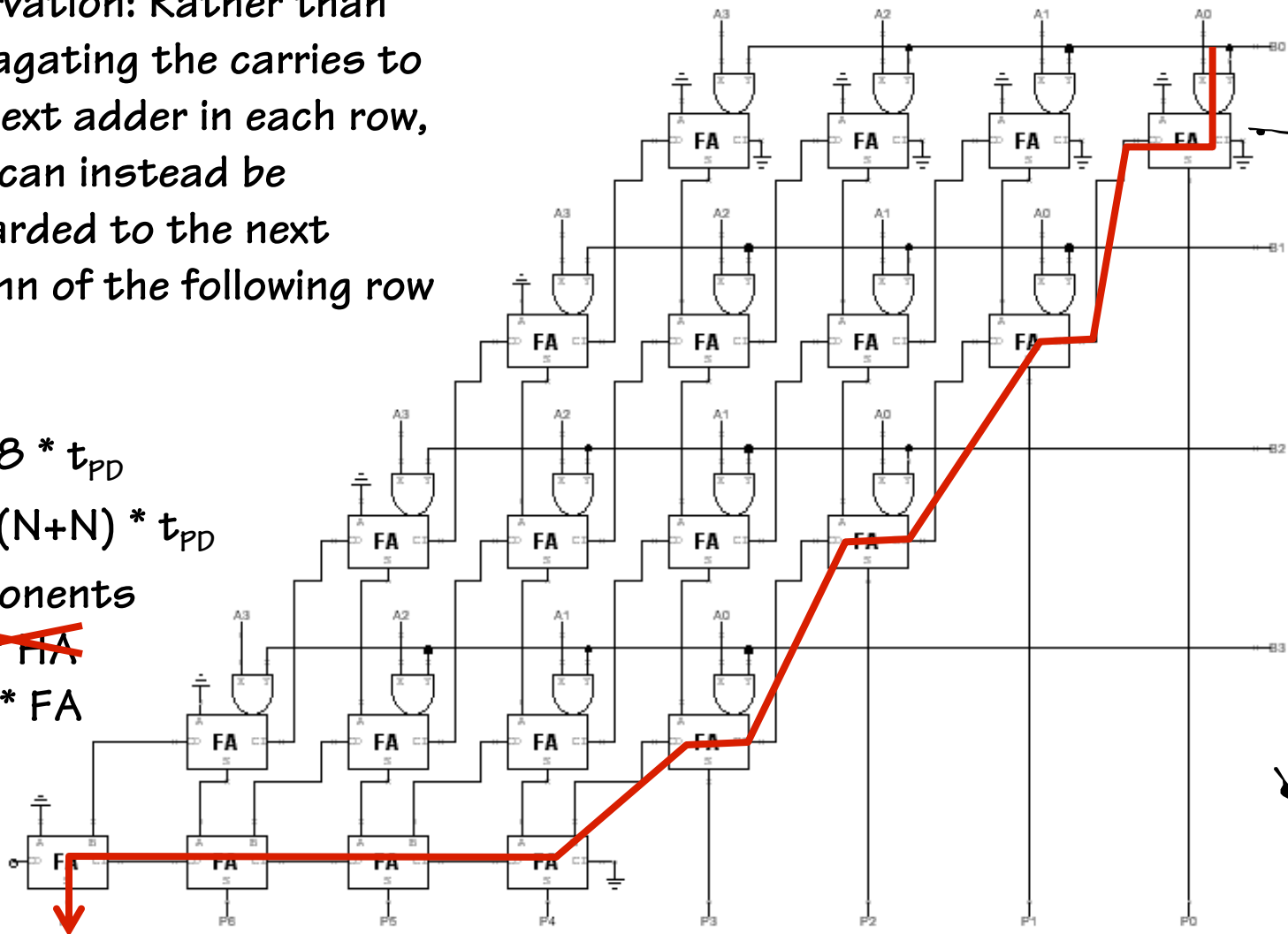


These Adders can be removed, and the AND gate outputs tied directly to the Carry inputs of the next stage.

This small performance improvement hardly seems worth the effort, however, this design is easier to "pipeline".



Higher-Radix Multiplication

 Idea: If we could use, say, 2 bits of the multiplier in generating each partial product we would **halve the number of rows and halve the latency of the multiplier!**



Booth's insight: rewrite $2*A$ and $3*A$ cases, leave $4A$ for next partial product to do!

$$\begin{aligned}
 B_{K+1,K} * A &= 0 * A \Rightarrow 0 \\
 &= 1 * A \Rightarrow A \\
 &= 2 * A \Rightarrow 2A \text{ or } 4A - 2A \\
 &= 3 * A \Rightarrow 4A - A
 \end{aligned}$$

Booth Recoding of Multiplier


current bit pair $\swarrow \searrow$ from previous bit pair \swarrow

B_{2K+1}	B_{2K}	B_{2K-1}	action	
0	0	0	add 0	
0	0	1	add A	
0	1	0	add A	
0	1	1	add 2*A	
1	0	0	sub 2*A	
1	0	1	sub A	$\leftarrow -2*A+A$
1	1	0	sub A	
1	1	1	add 0	$\leftarrow -A+A$

An encoding where each bit has the following weights:
 $W(B_{2K+1}) = -2 * 2^{2K}$
 $W(B_{2K}) = 1 * 2^{2K}$
 $W(B_{2K-1}) = 1 * 2^{2K}$

-89 = 10100111.0
 
$$\begin{aligned}
 &= -1 * 2^0 \quad (-1) \\
 &+ 2 * 2^2 \quad (8) \\
 &+ (-2) * 2^4 \quad (-32) \\
 &+ (-1) * 2^6 \quad (-64) \\
 \hline
 &-89
 \end{aligned}$$




Yep! Booth recoding works for 2-Complement integers, now we can build a signed multiplier.

A "1" in this bit means the previous stage needed to add 4*A. Since this stage is shifted by 2 bits with respect to the previous stage, adding 4*A in the previous stage is like adding A in this stage!

Booth Recoding

Logic surrounding
each basic adder:

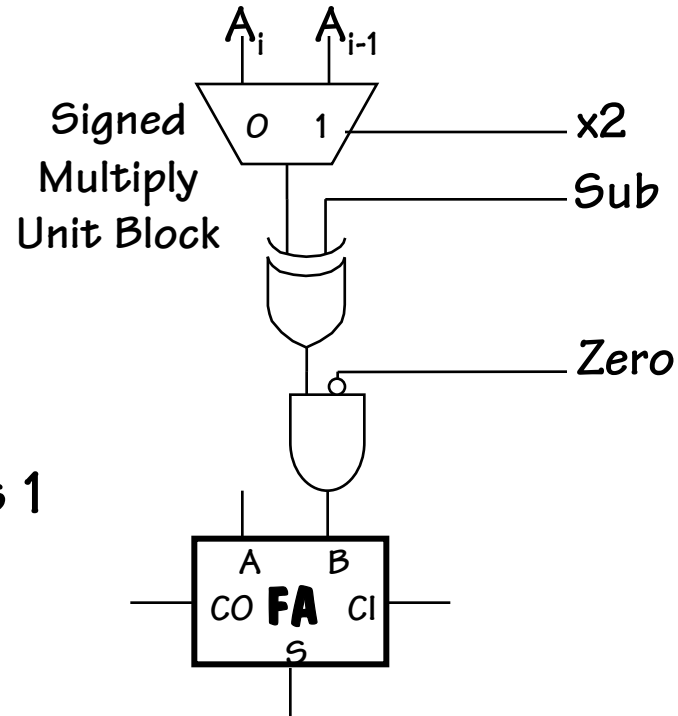- Control lines (x2, Sub, Zero) are shared across each row
- Must handle the "+1" when Sub is 1 (extra half adders in a carry save array)




NOTE:

- Booth recoding can be used to implement signed multiplications

B_{2K+1}	B_{2K}	B_{2K-1}	x2	Sub	Zero
0	0	0	X	X	1
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	X	X	1

Bigger Multipliers

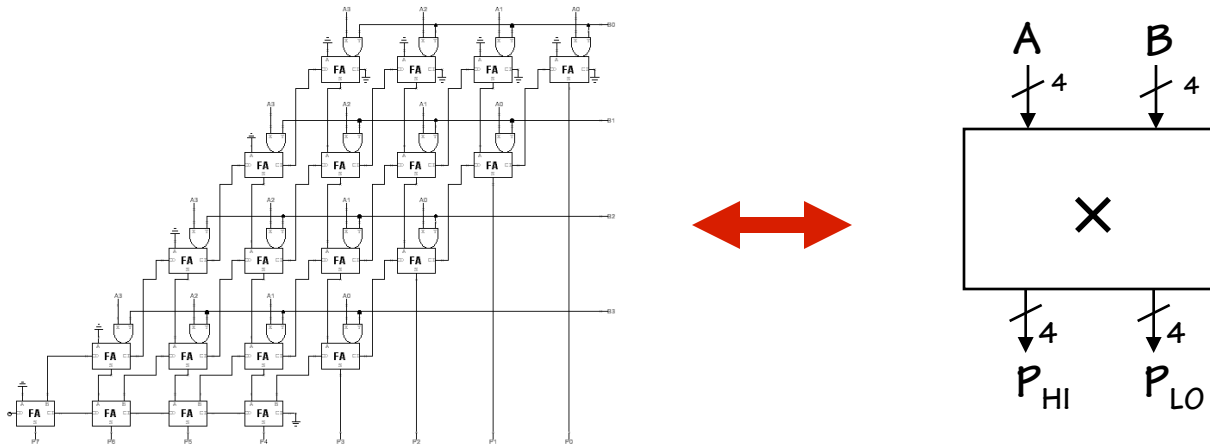- Using the approaches described we can construct multipliers of arbitrary sizes, by considering every adder at the “bit” level
- We can also, build bigger multipliers using smaller ones



- Considering this problem at a higher-level leads to more “non-obvious” optimizations


Can We Multiply With Less?

- How many operations are needed to multiply 2, 2-digit numbers?
- 4 multipliers
4 Adders
- This technique generalizes
 - You can build an 8-bit multiplier using 4 4-bit multipliers and 4 8-bit adders
 - $O(N^2 + N) = O(N^2)$

$$\begin{array}{r} A B \\ X C D \\ \hline D B \\ + A \\ + B \\ C A \\ \hline \end{array}$$

An $O(N^2)$ Multiplier In Logic

The functional blocks would look like

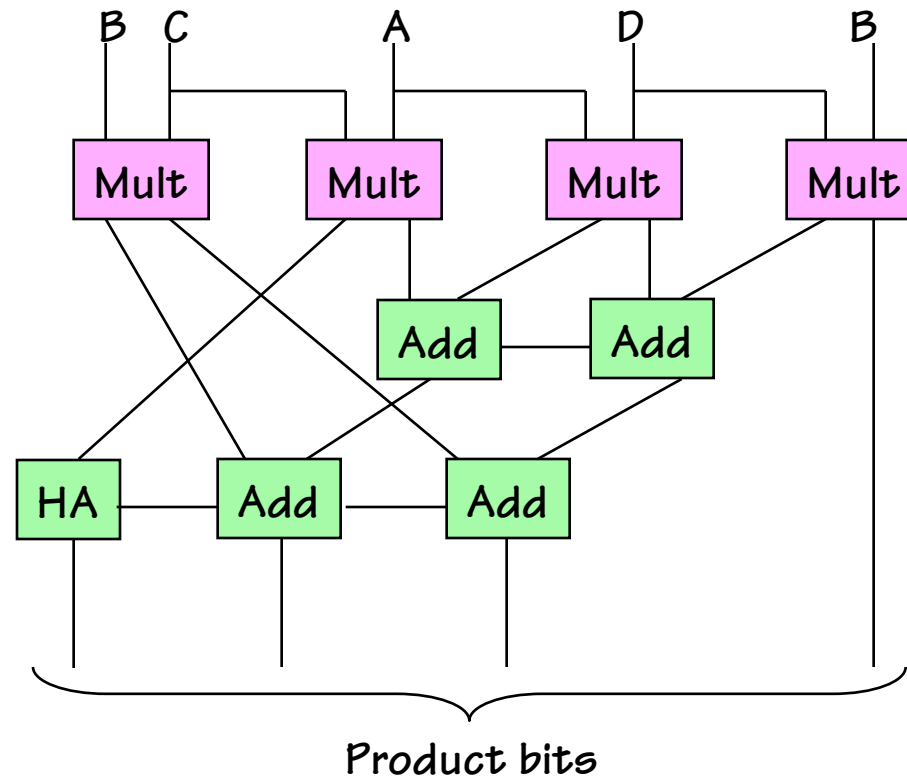

$$\begin{array}{r}
 AB \\
 \times CD \\
 \hline
 DB \\
 DA \\
 CB \\
 \hline
 CA
 \end{array}$$

A Trick

- The two middle partial products can be computed using a single multiplier and other partial products
- $DA + CB = (C + D)(A + B) - (CA + DB)$
- 3 multipliers
8 adders
- This can be applied recursively (i.e. applied within each partial product)
- Leads to $O(N^{1.58})$ adders
- This trick is becoming more popular as N grows. However, it is less regular, and the overhead of the extra adders is high for small N

$$\begin{array}{r}
 A\ B \\
 X\ \underline{C\ D} \\
 \quad DB \\
 \quad DA \\
 \quad CB \\
 \underline{CA}
 \end{array}$$

Let's Try it By Hand

1) Choose 2, 2 digit numbers to multiply $ab \times cd$

$$42 \times 37$$

2) Multiply $p_1 = a \times c$, $p_2 = b \times d$, $p_3 = (c + d)(a + b)$

$$p_1 = 4 \times 3 = 12, p_2 = 2 \times 7 = 14,$$


$$p_3 = (4+2)(3+7) = 60$$

3) Find partial subtracted sum, $SS = p_3 - (p_1 + p_2)$

$$SS = 60 - (12 + 14) = 34$$

 
4) Add to find product, $p = 100 * p_1 + 10 * SS + p_2$

$$p = 1200 + 340 + 14 = 1554 = 42 \times 37$$




An $O(N^{1.58})$ Multiplier In Logic

The functional blocks would look like

 

Where



$$SS = (C+D)(A+B) - (CA+DB)$$

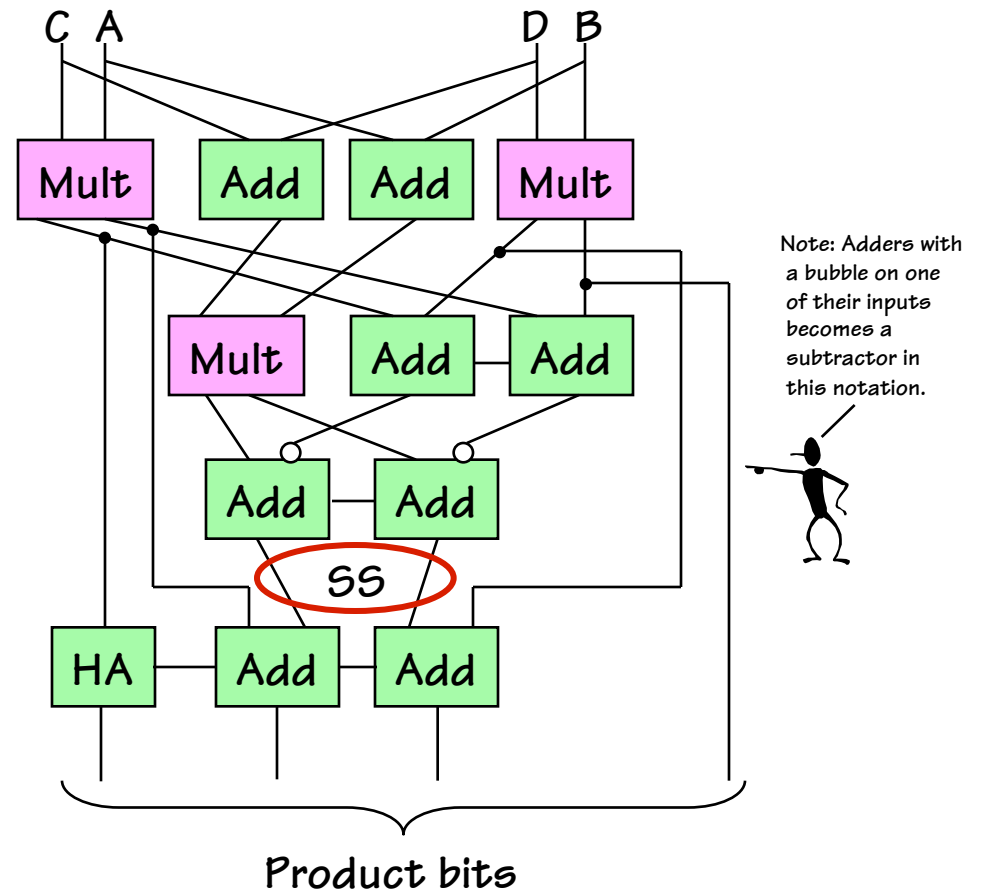


Binary Division

- Division merely reverses the process
 - Rather than adding successively larger partial products, subtract successively smaller divisors
 - When multiplying, we knew which partial products to actually add (based on the whether the corresponding bit was a 0 or a 1)
 - In division, we have to try **both ways**

Multiplication
Upside-down

  

Restoring Division

 

Division Example

Step 1:

$$\begin{array}{r} R \quad D \quad Q \\ 42 \div 7 = 6 \end{array}$$

Start:

$$\begin{array}{l} Q = 0 = 00000000 \\ R = 42 = 00101010 \\ D = (7*8) = 00111000 \end{array}$$

Note: K = 3, so repeat 4 times

Subtract:

$$\begin{array}{r} R = 42 = 00101010 \\ D = -(7*8) = 00111000 \\ \hline -14 = 11110001 \end{array}$$

Restore:

$$R = 42 = 00101010$$


Shifts:

$$\begin{array}{l} Q = 00000000 \\ D = 00011100 \end{array}$$

Step 2:

$$\begin{array}{r} R \quad D \quad Q \\ 42 \div 7 = 6 \end{array}$$

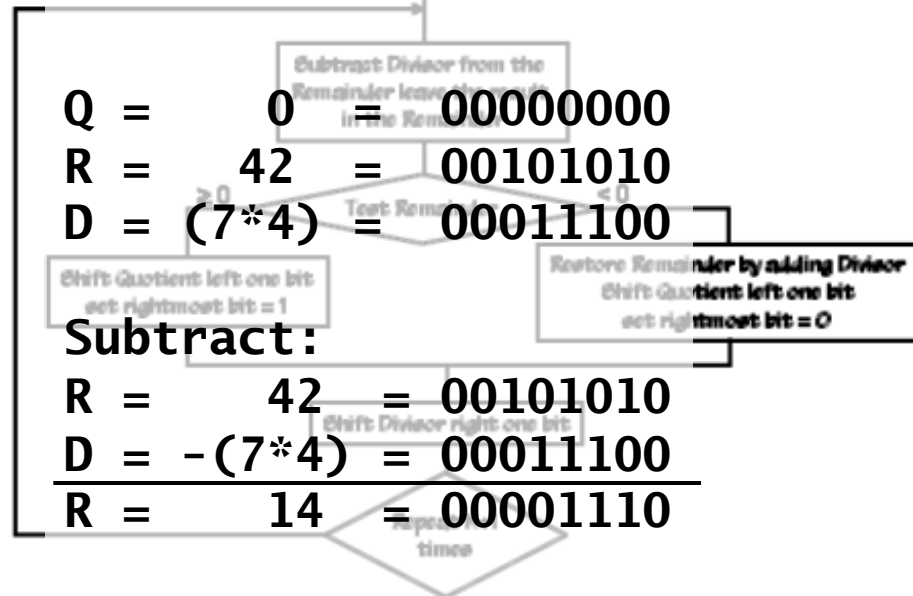Start: Align MSBs of Divisor and Remainder, K = number of bits shifted, Quotient = 0



Shifts:

$$\begin{array}{l} Q = 00000001 \\ D = 00001110 \end{array}$$

Division Example (cont)

Step 3:

$$\begin{array}{r} R \quad D \quad Q \\ 42 \div 7 = 6 \end{array}$$

$$\begin{array}{l} Q = 1 = 00000001 \\ R = 14 = 00001110 \\ D = (7*2) = 00001110 \end{array}$$

Subtract:

$$\begin{array}{r} R = 14 = 00001110 \\ D = -(7*2) = 00001110 \\ \hline 0 = 00000000 \end{array}$$


No Restore
Shifts:

$$\begin{array}{l} Q = 00000011 \\ D = 00000111 \end{array}$$

Step 4:

$$\begin{array}{r} R \quad D \quad Q \\ 42 \div 7 = 6 \end{array}$$

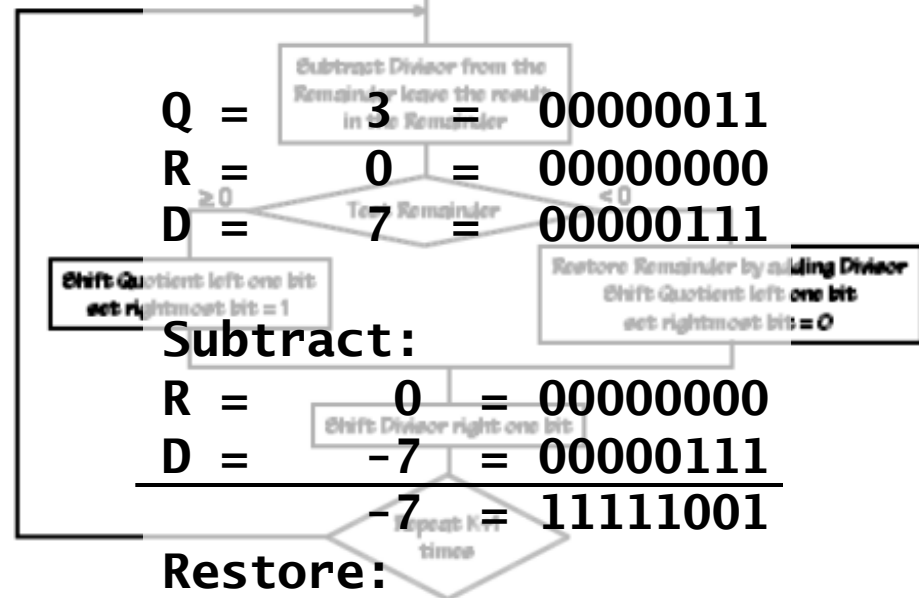Start: Align **MIDDLE** of Divisor and Remainder, K = number of bits shifted, Quotient = 0



$$\begin{array}{l} Q = 3 = 00000011 \\ R = 0 = 00000000 \\ D = 7 = 00000111 \end{array}$$

Subtract:

$$\begin{array}{r} R = 0 = 00000000 \\ D = -7 = 00000111 \\ \hline -7 = 11111001 \end{array}$$

Restore:

$$R = 0 = 00000000$$

Shifts:

$$\begin{array}{l} Q = 00000110 \\ D = 00000111 \\ R = 00000000 \end{array}$$


Division Big Boxes

We can use this algorithm to design a combinational divider. It takes as inputs a divisor, R , a dividend, D , and outputs a quotient and a remainder.

Dividing is generally slower than multiplication.

The worst case propagation delay waits for every adder stage to generate its most significant bit, thus, each stage has to wait for the full sum from the previous stage to complete.

One quotient-bit per adder stage

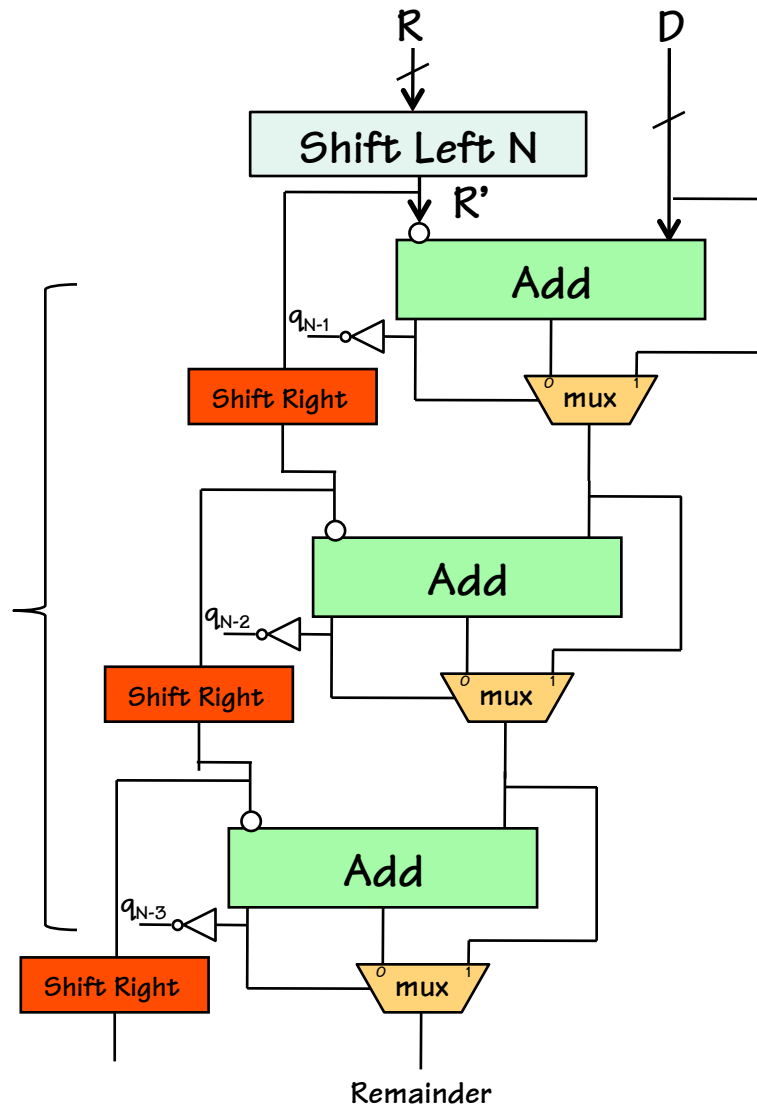

Next Time

- We dive into floating point arithmetic

