 


### Problem 1.


In the follows answers, the black section of the circuit is the new section, while the grey section is the section that was given in the problem.

a)




A	B	C	D	y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

b)

 

A	B	C	D	y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

c)

 

A	B	C	y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

## Problem 2.


The basic approach to solving logic problems is to apply a process of systematic elimination (i.e. eliminate impossible outputs for a given combination of inputs).

a) First consider those functions that can be implemented using only an inverting 2-input mux. The truth table for such a mux is shown on the right with the inputs labeled according to the given variables.

K	J	I	Output
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


For example, in the first row the output of function E is 0. In order to generate this value, either one of I or J must be 1 (hence neither can be connected to X, Y, or Z) or input I must be tied to 1 if any of X, Y or Z are connected to K, or both J and K are connected to 1.

 Likewise, the only way E could output a 1 when the 3 inputs are 1s (last row) is if J is tied to a 0.




K=Z, I=X, J=Y yields function C

 b) Using similar elimination method as in part a), it can be found the E is the only possible result.




c) Only function A can be implemented as a single-level CMOS gate.

Function A, as follows:

 

 d) An implementation of function E can be used to compute function B with the following circuit, if the unknown input, U, is properly connected.



What signal should be connected to U? X

Problem 3.

- a) Give binary values for  $I_0, I_1, I_2,$  and  $I_3$  which implement the following functions on the two inputs A and B: AND(A,B), OR(A,B), XOR(A,B), NAND(A,B), and NOR(A,B) (2 pts).


Gate	$I_0$	$I_1$	$I_2$	$I_3$
AND(A,B)	0	0	0	1
OR(A,B)	0	1	1	1
XOR(A,B)	0	1	1	0
NAND(A,B)	1	1	1	0
NOR(A,B)	1	0	0	0

- b) Can every 2-input Boolean function be implemented using Ben's structure? Explain why or why not. (2 pts)

Every 2-input Boolean function can be implemented using a 4 input mux by connecting the two inputs to the select lines and copying the function's truth table values to their corresponding input.

 
- c) Show how to implement an inverter, as well as every 2-input gate using no more than 2-multiplexers to construct each one. (16 points)

An inverter can be implemented using a two input mux as follows:




All other gates can be implemented using no more than 2 muxes as follows (using the inverter implementation shown above):


Zero		
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	0

 


B		
A	B	Y
0	0	0
0	1	1
1	0	0
1	1	1

 


AND		
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 


XOR		
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

 


A > B		
A	B	Y
0	0	0
0	1	0
1	0	1
1	1	0

 


OR		
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 


A		
A	B	Y
0	0	0
0	1	0
1	0	1
1	1	1

 


NOR		
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 


B > A		
A	B	Y
0	0	0
0	1	1
1	0	0
1	1	0

 


XNOR		
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

 


NOT B		
A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0

 


B ≥ A		
A	B	Y
0	0	1
0	1	1
1	0	0
1	1	1

 


A ≥ B		
A	B	Y
0	0	1
0	1	0
1	0	1
1	1	1

 


NAND		
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 

NOT A		
A	B	Y
0	0	1
0	1	1
1	0	0
1	1	0

 

ONE		
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	1

 

d) Explain how every 4-input Boolean function can be implemented with an 8-input mux and a single inverter.



For the 4-input function  $f(A,B,C,D)$ , we can choose  $A$ ,  $B$ , and  $C$  to be the select inputs of the 8-input mux. With this arrangement, each of the 8 data inputs can be set to one of four values:  $0$ ,  $1$ ,  $D$ , and  $\overline{D}$ . (We can obtain the value of  $\overline{D}$  using the single inverter given to us.) To determine which of the four values a data input should be attached to, one can examine the two corresponding rows for a given  $A, B, C$  combination in the truth table. If both values are  $0$ , then the corresponding mux input is connected to  $0$ . Similarly, if both values are  $1$  the mux input is set to one. If the two outputs for a given  $A, B, C$  combination are a  $0$  and a  $1$ , then they must either follow  $D$  or  $\overline{D}$ , and the mux input should be connected accordingly.

e) The TA explains to Lee that no more than 40% of all 4-input Boolean functions can be implemented with only an 8-input mux (i.e. no inverter). He jots down an upper bound on the number of such functions:  $3^8/2^{14}$ . Can you explain the TA's reasoning?

With no inverter, each of the mux's data inputs can be set to one of only three possible values:  $0$ ,  $1$ , and  $D$ . As a result, there are  $3^8$  permutations of inputs to this mux, so only  $3^8$  Boolean functions can be implemented in this configuration. However, instead of using  $D$  as a possible data input, we can swap  $D$  with one of the three select inputs ( $A$ ,  $B$ , or  $C$ ). (This allows some functions that would have used  $\overline{D}$  as a data input – functions where  $D=1$  leads to  $f=0$  and  $D=0$  leads to  $f=1$ .) By choosing to use either  $A$ ,  $B$ ,  $C$ , or  $D$  as the data input, there are  $3^8 * 4$  possible functions that can be implemented (Some of these functions are the same, so  $3^8 * 4$  is an upper bound). Since there are a total of  $2^{16} = 2^{2^4}$  possible 4-input Boolean functions, an upper bound on the percentage of 4-input functions that can be implemented using an 8-input mux without an inverter is  $[(3^8 * 4) / 2^{16}]$ , which is about 40%.
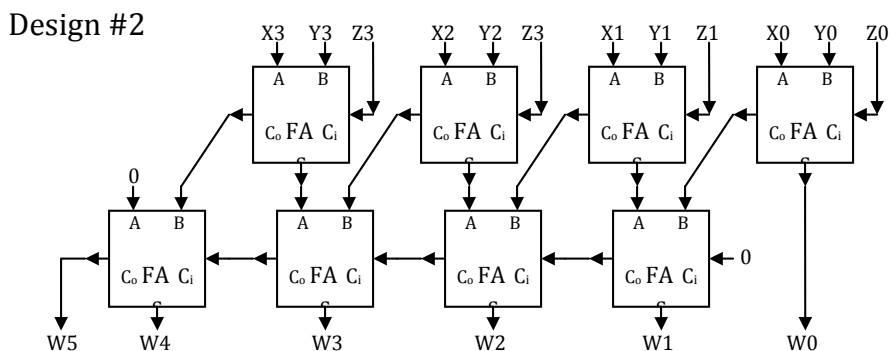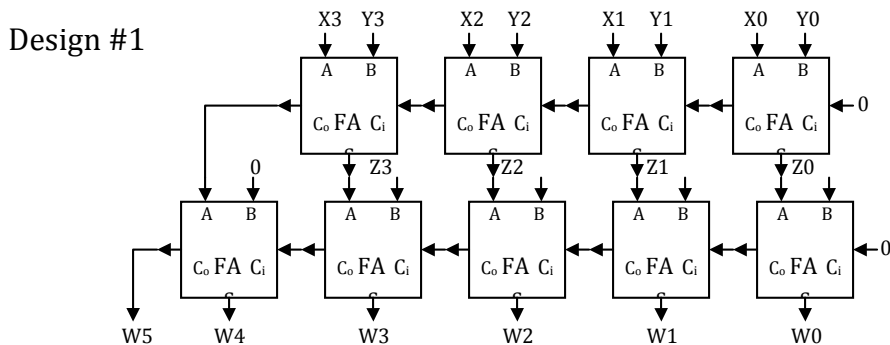
## Problem 4)

Consider the follow two circuits for adding 3, 4-bit numbers (i.e.  $W = X + Y + Z$ ):



- a) Ignoring the speed of the calculation, do both 3-input adder designs compute the same result? If not, how do they differ? (5 pts)

Yes, they both compute the same result

- b) Assume a unit delay for each full-adder (i.e. the output will become valid one time unit after all inputs are valid). Which design computes all bits of the sum fastest? Which design computes the first (least-significant) bit fastest? (5 pts)

By following the path of maximum delay in both circuits, one finds that Design #1 takes 6 unit delays in the worst case, and Design #2 takes 5 unit delays in the worst case. Also, Design #1 takes 2 unit delays to compute first bit, and Design #2 takes 1 unit delay to compute first bit.

- c) Obviously, design #1 uses one more adder than design #2. Explain how design #1 can be modified slightly to use one fewer full-adder. After this change, which design computes all bits of its sum fastest? (5 pts)

Eliminate rightmost adder on bottom row of Design #1 and connect  $Z_0$  to the carry input of the rightmost adder on the top row, instead of 0.

- d) Both designs could be improved by incorporating carry-lookahead logic in place of their carry-propagation chains. Which design would require less logic to implement carry lookahead? Explain. (5 pts)


Compare number of carry-propagation chains. Since Design #1 has two and Design #2 has one, Design #2 would require less logic (lesser change) since only one chain has to be fixed.

- e) Modify both designs to support the following operations:

$$W = X + Y + Z \quad \text{or} \quad W = X + Y - Z,$$

based on the value of a control signal (CTRL). (5 pts)

 In each design, replace inputs connected to  $Z_i$  with:



Also, in the first design connect the carry-in of the upper right adder (currently connected to 0) to CTRL.

In the second design a half-adder need to be added, that adds CTRL to the output of the first adder (with output labeled *WO*). The sum of this adder will be the new “*WO*” and the carry will be fed into the first adder in the second row, which currently is connected to a ‘0’.